

## Practice Questions (and Answers) for Final Exam

### CS 64, Winter 2020, Matni

**IMPORTANT NOTE:** These questions are NOT representative of EVERYTHING you need to study for the midterm exam! You should also review your lab assignments questions and also all the examples and demos done in class.

1. Binary-to-decimal/hexadecimal conversion
  - a. Convert **1001 0010 1100 0011** to 4-digit hexadecimal
  - b. Convert the *signed* binary value **1001 1111** to decimal
2. Add the 2 following 8-bit numbers: **0110 0010** and **0011 0100** and indicate the status of the carry and overflow bits at the end of the addition. Interpret your findings.
3. Translate this MIPS assembly code into C/C++ code.

```
.data
talk: .asciiz "blabla"
cs: .word 3
.text
main:
    li $t0, 5
    la $t1, cs
    lw $t2, 0($t1)
    blt $t0, $t2, gothere
    li $v0, 4
    la $a0, talk
    syscall
    j end
gothere:
    li $v0, 4
    la $a0, talk
    syscall
    syscall
end:
    li $v0, 10
    syscall
```

4. Write the following MIPS instructions in machine-language hexadecimals (show all work): **addiu \$t0, \$s0, 17** and **sub \$v0, \$s4, \$t5**
5. Given a MIPS machine language instruction of **0x02088024**, and being told that it is an R-type, what is the assembly instruction?
6. What will the final value in register \$s0 in this code be?

```
li $s0, 20
sll $s0, $s0, 2
add $s0, $s0, $s0
sra $s0, $s0, 4
```

7. Consider the C/C++ code below:

```
// arr is a globally accessible array of ints
// s0 already holds a value of type unsigned int
unsigned int s1 = arr[s0];
unsigned int s2 = arr[s0 - 1];
unsigned int s3 = arr[s0 + 1];
```

Using **no more than six instructions**, implement the above code snippet in MIPS. You **don't** have to follow the MIPS Calling Convention.

8. Consider the C/C++ code below.

```
int sum( int arr[], int size )
{
    if ( size == 0 )
        return 0;
    else
        return sum( arr, size - 1 ) + arr[size - 1];
}
```


- Knowing that you **have to follow the MIPS Calling Convention**, which variables should be preserved either directly (via the stack) or indirectly (in an S-register) in order to maintain the intended program behavior?
- Implement the previously shown C/C++ code using MIPS assembly, taking care to preserve the values you identified previously. Ignore the **.data** part and just focus on the **.text** part of the program.

9. Show how a NOR function can be used as an AND function.
10. Simplify this expression using Boolean algebra:  $F = \text{NOT} ((A \text{ NOR } B) \cdot (C + A \cdot B))$  and draw the resulting circuit.
11. Consider the following truth table, which includes don't cares:

A	B	C	D	R
0	0	0	0	1
0	0	0	1	0
0	0	1	0	X
0	0	1	1	0
0	1	0	0	X
0	1	0	1	1
0	1	1	0	X
0	1	1	1	X
1	0	0	0	X
1	0	0	1	0
1	0	1	0	1
1	0	1	1	X
1	1	0	0	1
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

Simplify the output function **R** using a Karnaugh Map, and show the resulting sum-of-products representation. Show the map, along with the boxes you chose. For full credit, both the number of ORs (+) and the sizes of the products must be minimal.

12. Consider this circuit:

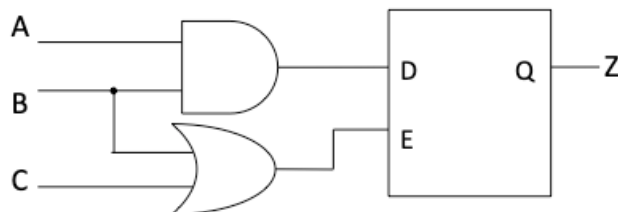

What does the output **Z** do with the following values of A, B, and C (suppose that these values happen in sequence: that is one after the other as shown in the table). Also explain why:

A	B	C	Z	Reason
0	0	1		
1	1	0		
0	0	0		
1	0	0		
1	0	1		

Practice Questions for CS64 (W20) Final Exam

13. Consider a device that consists of three buttons labeled “UP” and “RESET”, along with a light. The device internally counts the number of times “UP” is pressed, and when it is pressed two times, the device causes the light to illuminate. Additional presses of “UP” do nothing. Pressing “RESET” at any point will reset the internal counter back to zero, and will cause the light to go out. (Note that the light may have already been off, as when the user presses “UP” once followed by “RESET”.)

For this question, you will implement this device as a finite state machine. The machine has the following two external inputs:

R: set to 1 whenever “RESET” is pressed

U: set to 1 whenever “UP” is pressed


The machine also has one external output:

L: set to 1 whenever the light should be illuminated


If both “RESET” and “UP” are pressed at the same time, then the behavior should be as if only “RESET” was pressed. Basically, if R is set, no matter what state you are in, you go back to the initial state. If R is set, we even assume the light will turn off.

- a) Draw the finite state machine diagram corresponding to this task. All transitions should be drawn as products of R and U. For example, if a particular transition should be taken only if  $R = 1$  and  $U = 0$ , then this should be drawn as  $R.\bar{U}$  or  $R.!U$ .
- b) How many D-FFs are necessary to implement this state machine?
- c) If we used the “one-hot” method, how many D-FFs are now necessary?
- d) Draw the truth table for all the states, showing current state bits, input bits R and U, next state bits, and output bit L. If there are “non-applicable” states, you should show them in this truth table.
- e) Using K-Maps, write the optimal functions for the next state bits and the output.

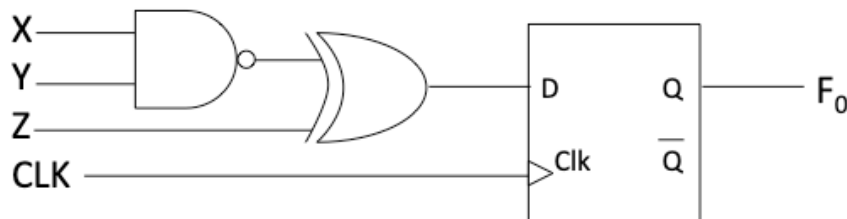14. Consider the following digital circuit:



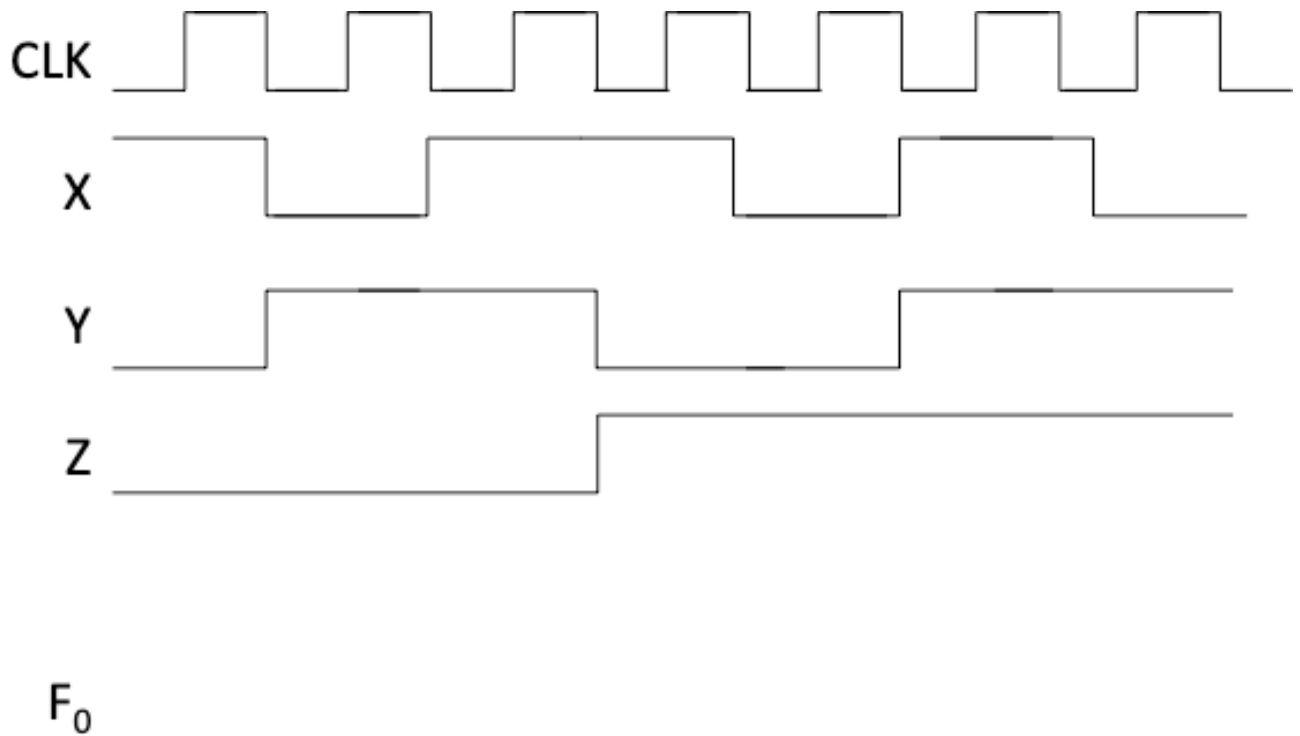- Write the expression for the next-state bit  $F_0$  as a sum-of-product.
- Assuming that  $F_0$  is initially 0, complete the timing diagram for  $F_0$  based on your answer above. Make your drawing as accurate as you can. You can show intermediate variable values if you want as well.



**\*\*\* TO GET THE MOST OUT OF THIS REVIEW, DO THE QUESTIONS FIRST BEFORE LOOKING AT THE ANSWERS!\*\*\***

**ANSWERS TO THE REVIEW QUESTIONS FOR FINAL EXAM**

1.
  - a. 1001 0010 1100 0011 /bin = 0x92C3
  - b. 1001 1111 /bin  $\rightarrow$  0110 0000 + 1 = 0110 0001 =  $-(2^6 + 2^5 + 1) = -97$
  
2.   0110 0010  
      + 0011 0100  
      1001 0110  
 The carry out bit = 0, the overflow bit is 1.  
 So, if these were 2 unsigned numbers, there would be no carry out, but if these were 2 signed numbers, then we'd have overflow.
  
3. In C/C++:  
 char talk[] = "blabla";  
 int cs = 3;  
 int t0 = 5;  
 if (t0 >= cs) { printf(talk); }  
 else { printf(talk); printf(talk); }
  
4. **addiu \$t0, \$s0, 17** = 0x26080011  
    **sub \$v0, \$s4, \$t5** = 0x028D1022
  
5. **0x02088024**       =       and \$s0, \$s0, \$t0
  
6. \$s0 = 20                     $\rightarrow$  This is in decimal. So it's 0000 ... 0001 0100 (in 32-bit binary)  
    sll \$s0, \$s0, 2            $\rightarrow$  \$s0 becomes 0000 ... 0101 0000  
    add \$s0, \$s0, \$s0        $\rightarrow$  \$s0 becomes 0000 ... 1010 0000  
    sra \$s0, \$s0, 4            $\rightarrow$  \$s0 becomes 0000 ... 0000 1010 = **10 /dec**
  
7. In 6 or fewer instructions:  
    la \$t0, arr  
    sll \$s0, \$s0, 2  
    addu \$t0, \$t0, \$s0  
    lw \$s1, 0(\$t0)  
    lw \$s2, -4(\$t0)  
    lw \$s3, 4(\$t0)

8. We assume **arr** is in **\$a0** and **size** is in **\$a1**.

```
.text
sum:
    addiu $sp, $sp, -12 # PUSH
    sw $ra, 8($sp)
    sw $s1, 4($sp)
    sw $s0, 0($sp)

    li $v0, 0
    beq $a1, $zero, return    # is size !=0?

    addi $a1, $a1, -1    # size is now: size - 1
    move $s0, $a0        # preserve &a0
    move $s1, $a1        # preserve a1 (size)

    jal sum              # recursive call

    sll $s1, $s1, 2      # multiply size by 4
    add $s0, $s0, $s1    # s0 is now the address of a[size-1]

    lw $t0, 0($s0)      # Get that array element
    add $v0, $v0, $t0    # add it to $v0

return:
    lw $ra, 8($sp)      # POP
    lw $s1, 4($sp)
    lw $s0, 0($sp)
    addiu $sp, $sp, 12
    jr $ra

main:
    la $a0, arr         # a0 = &a[]
    li $a1, 4           # a1 = size

    jal sum


exit:
    li $v0, 10
    syscall
```

```
int sum( int arr[], int size ) {
    if ( size == 0 )
        return 0 ;
    else
        return sum( arr, size - 1 ) + arr[size-1]; }
```

9. Taking advantage of DeMorgan's theorem, you will not that if the inputs to the NOR are inverted, you get:  $F = \text{NOT}(\bar{A} + \bar{B}) = A.B$

Practice Questions for CS64 (W20) Final Exam

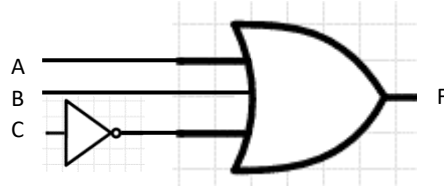10.  $F = \text{NOT}((A \text{ NOR } B) \cdot (C + A \cdot B))$   
 $= \text{NOT}((\bar{A} \cdot \bar{B}) \cdot (C + A \cdot B))$   
 $= \text{NOT}(\bar{A} \cdot \bar{B} \cdot C + \bar{A} \cdot \bar{B} \cdot A \cdot B)$   
 $= \text{NOT}(\bar{A} \cdot \bar{B} \cdot C)$   
 $= A + B + \bar{C}$



11. K-Map:

CD \ AB	00	01	11	10
00	1	X	1	X
01		1	X	
11		X	X	X
10	X	X	X	1

Since X's can be either 0 or 1, to maximize the size of our groupings and minimize the number of our groupings, we can transform the above to the following with 2 major groupings:

CD \ AB	00	01	11	10
00	1	1	1	1
01		1	1	
11		1	1	0
10	1	1	1	1

This gives us the formula:  $F = \bar{D} + B$

**NOTE:** I purposely made one of the Xs into a 0, so that I could minimize my groupings.


12.

A	B	C	Z	Reason
0	0	1	0	D-latch is enabled ( $E = 1$ ). $D = 0$ , so $Q = 0$ .
1	1	0	1	D-latch is enabled ( $E = 1$ ). $D = 1$ , so $Q = 1$ .
0	0	0	1	D-latch is not enabled ( $E = 0$ ). So $Q = Q_{old} = 1$ .
1	0	0	1	D-latch is not enabled ( $E = 0$ ). So $Q = Q_{old} = 1$ .
1	0	1	0	D-latch is enabled ( $E = 1$ ). $D = 0$ , so $Q = 0$ .



## 13. State diagram:

a.

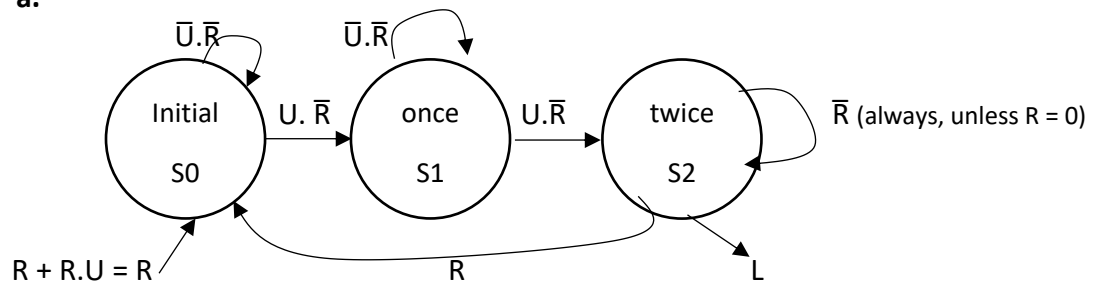

- b. We have 3 states, so we'd need 2 bits. Let's call them B1 and B0. This would require 2 D-FFs.
- c. Using the "one-hot" method, we'd need a bit/D-FF for each state, i.e. 3 D-FFs.
- d. S0 would be B1B0 = **00**, S1 would be **01**, S2 would be **10**. The combination of B1B0 = **11** is undefined. The state diagram/truth table is:

inputs				outputs		
B1	B0	U	R	B1*	B0*	L
0	0	0	0	0	0	0
0	0	1	0	0	1	0
0	1	0	0	0	1	0
0	1	1	0	1	0	0
1	0	X	0	1	0	1
X	X	X	1	0	0	0

e. K-Maps for every output:

**For B1\*:**

B1B0	00	01	11	10
UR				
00				<b>1</b>
01				
11				
10		<b>1</b>		<b>1</b>

**For B0\*:**

	00	01	11	10
UR				
00		<b>1</b>		
01				
11				
10	<b>1</b>			

**For L:**

	00	01	11	10
UR				
00				<b>1</b>
01				
11				
10				<b>1</b>

$$B1^* = !B1.B0.U.!R + B1.!B0.!R$$

$$B0^* = !B1.B0.!U.!R + !B1.!B0.U.!R$$

$$L = B1.!B0.!R$$

14.

a.  $F_0 = !(X.Y) \text{ XOR } Z = (X.Y).Z + !(X.Y).!Z = XYZ + !X!Z + !Y!Z$

NOTE 1:  $F_0$  changes its value ONLY on the rising edge of CLK (hence the dotted lines in the diagram below – it's helpful if you show those). Remember that is because  $F_0$  is the result of sequential logic (it's an output of a D-FF).

NOTE 2: Since  $F_0$  is a combination of  $!(X.Y)$  and  $Z$ , it's helpful (and makes easier to draw the  $F_0$  diagram) to show the timing diagram for  $!(X.Y)$  by itself. Remember that  $!(X.Y)$  is combinatorial logic, so it doesn't rely on CLK edges.

